 


Logic Gates

1. Timing Issues
2. Specifying Logic Functions
3. Logic Design




Handouts: Lecture Slides

1

Combinational Devices

Static discipline

- A **combinational device** is a circuit element that has
- one or more digital **inputs**
 - one or more digital **outputs**
 - a **functional specification** that details the value of each output for every possible combination of valid input values
 - a **timing specification** consisting (at minimum) of an upper bound t_{pd} on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values

 

2

A Combinational Digital System




- A set of interconnected elements is a combinational device if
 - each circuit element is combinational
 - every element input is connected to exactly one element output or 1 (power supply) or 0 (ground)
 - the circuit contains no directed cycles
- Why is this true?
 - Given an acyclic circuit meeting the above constraints, we can derive functional and timing specs for the input/output behavior from the specs of its components!



3

Signal Timing: Propagation Delay

 
Propagation delay t_{pd} is upper bound between new valid inputs and new valid output



4

Signal Timing: Contamination Delay

 Contamination delay t_{cd} is lower bound between invalid inputs and invalid output




Do we really need t_{cd} ?

Usually not... it'll be important when we design circuits with registers (coming soon!)

If t_{cd} is not specified, safe to assume it's 0.

5

Timing Analysis

 

Logically valid A, B \rightarrow Logically valid C (static discipline)


$t_{pd} = 5$ $t_{cd} = 1$ for each NAND gate

Over all input combinations, over all input-output paths

What is the propagation delay for the circuit?
What is the contamination delay for circuit?

6

Logical Analysis

 


Logic Function?

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

7

Combinational Contract Summary




$A \text{ --- } \text{NAND} \text{ --- } B$

A	B
0	1
1	0

t_{PD} propagation delay

t_{CD} contamination delay

 


Note:

1. No Promises during XXXXXX
2. Default (conservative) spec: $t_{CD} = 0$

8

Oh yeah... one last issue

 


- Recall the rules for *combinational devices*:

Output guaranteed to be valid when **all** inputs have been valid for at least t_{PD} , and, outputs may become invalid no earlier than t_{CD} after an input changes!

Many CMOS gate implementations adhere to even tighter restrictions.

9

What happens in this case?

 

- LENIENT** Combinational Device:

Output guaranteed to be valid when **any** combination of inputs sufficient to determine output value has been valid for at least t_{PD} . *Tolerates transitions -- and invalid levels -- on irrelevant inputs!*

NOR:	<table> <tr><th>A</th><th>B</th><th>Z</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	A	B	Z	0	0	1	0	1	0	1	0	0	1	1	0	<i>Lenient</i> NOR: <table> <tr><th>A</th><th>B</th><th>Z</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>x</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>x</td><td>0</td></tr> </table>	A	B	Z	0	0	1	x	1	0	1	x	0	
A	B	Z																												
0	0	1																												
0	1	0																												
1	0	0																												
1	1	0																												
A	B	Z																												
0	0	1																												
x	1	0																												
1	x	0																												

10

How do we specify what we want?

Truth Tables

k inputs

output

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

2^k rows

input combination

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	1	0	1
1	1	1	1

Assume unspecified input combinations produce 0

Number of Distinct truth tables with k inputs is 2^{2^k}

11

Truth Tables and Logic Equations

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	1	0	1

$F = 1$ if $A=0$ AND $B=0$ AND $C=0$ OR $A=0$ AND $B=0$ AND $C=1$ OR $A=0$ AND $B=1$ AND $C=0$ OR $A=0$ AND $B=1$ AND $C=1$ OR $A=1$ AND $B=1$ AND $C=0$

$F = 0$ otherwise

Write as a logic equation:

$$F = \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot \bar{C}$$


or

$$F = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} B \bar{C} + \bar{A} B C + A B \bar{C}$$

12

Logic Equations and AND-OR Circuits
 
$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$$




13

No problem...

- DeMorgan's laws

$$\bar{A} + \bar{B} = \overline{AB} \quad \bar{A}\bar{B} = \overline{A+B}$$


- NAND and NORs are universal

 

14

NAND-NAND Circuit
 
$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$$



Number of transistors if implemented in CMOS: 40
(ignoring input inverters)

15

Identities for Logic Functions

Given logic functions f, g, h

$$\begin{aligned} f \cdot f &= f & f + f &= f \\ f \cdot 1 &= f & f + 1 &= 1 \\ f \cdot 0 &= 0 & f + 0 &= f \\ f \cdot \bar{f} &= 0 & f + \bar{f} &= 1 \end{aligned}$$

Distributive laws

$$\begin{aligned} f \cdot (g + h) &= f \cdot g + f \cdot h \\ (f + g) \cdot (f + h) &= f + g \cdot h \quad \text{WHY?} \end{aligned}$$

16

Simplifying Logic Equations

Apply identities to simplify equation for F


$$\begin{aligned}
 F &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} \\
 &= \bar{A}\bar{B} + \bar{A}B + A\bar{B}\bar{C} \\
 &= \bar{A} + A\bar{B}\bar{C}
 \end{aligned}$$

Can we simplify further?

17

Comparison
 
$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$$



40 Transistors

8 Transistors

18

Parity (XOR) Functions

Count the number of 1's in the inputs and produce a 1 if odd

A	B	P ₂
0	1	1
1	0	1

A	B	C	P ₃
0	0	1	1
0	1	0	1
1	0	0	1
1	1	1	1

Smallest AND-OR circuit for P_n will contain 2^{n-1} AND gates

Similar increase for adders, subtractors, multipliers, and most arithmetic functions

19

Combinational Composition


Suppose we have some 2-input XOR gates:



$$\begin{aligned}
 t_{pd} &= 1 \\
 t_{cd} &= 0
 \end{aligned}$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

And we want an N-input XOR:

 


$$t_{pd} = O(N) \text{ -- WORST CASE.}$$

output = 1
iff number of 1s
input is ODD
("ODD PARITY")

Can we compute N-input XOR faster?

20

 *I think that I shall never see
a circuit lovely as...*




N -input TREE has $O(\log_2 N)$ levels.

Signal propagation takes $O(\log_2 N)$ gate delays.

21

Logic Geek Party Games

 - You have plenty of ANDs and ORs, but only 2 inverters. Can you invert more than 2 independent inputs?



- CHALLENGE:** Come up with a combinational circuit using ANDs, ORs, and at most 2 inverters that inverts A, B, and C !
- Such a circuit exists. What does that mean?
 - If we can invert 3 signals using 2 inverters, can we use 2 of the pseudo-inverters to invert 3 more signals?
 - Do we need only 2 inverters to make ANY combinational circuit?
- Hint: Is our 3-inv device *LENIENT*?

22